

Hanoi University of Science and Technology
School of Engineering Physics

LAB REPORT

For Electrics and Thermodynamics

PH1026

Experiment 1

Student name : Nguyen Viet Anh
Student ID : 20150143
Group number : 1

Experiment 1**Measurement of Resistance, Capacitance, Inductance and Resonant Frequencies of RLC using Oscilloscope****1. Measurement of resistance, capacitance, and inductance****a. Measurement of unknown resistance**

f (Hz)	R₀ (Ω)	R_x (Ω)	ΔR_x (Ω)
500	332.0	332.0	0.3
1000	332.0	332.0	0.3
1500	331.0	331.0	0.7
		$\overline{R_X} \approx 331.7$	$\overline{\Delta R_X} \approx 0.4$

$$s.d._{Rx} = \sqrt{\frac{\sum_{i=1}^3 (R_{Xi} - \overline{R_X})^2}{3}} \approx 0.5(\Omega)$$

$$S.D._{Rx} = \Delta R_X = \frac{s.d.}{\sqrt{n}} \approx 0.3(\Omega)$$

$$\text{Result: } R_X = \overline{R_X} \pm \Delta R_X = 331.7 \pm 0.3(\Omega)$$

b. Measurement of unknown capacitance

f (Hz)	Z_c = R₀ (Ω)	ΔZ_c (Ω)	C_x = $\frac{1}{2\pi f R_0}$ (μF)
1000	154.0	154.0	1.033
2000	78.0	78.0	1.020
3000	52.0	52.0	1.020
			$\overline{C_x} \approx 1.024$

$$s.d._{Cx} = \sqrt{\frac{\sum_1^3 (\overline{C_x} - C_i)^2}{3}} \approx 0.006(\mu F)$$

$$S.D._{Cx} = \frac{s.d.}{\sqrt{n}} = \frac{0.006}{\sqrt{3}} \approx 0.003(\mu F)$$

Result: $C_X = \overline{C_X} \pm \Delta C_X = 1.024 \pm 0.003 \text{ (}\mu\text{F)}$

c. Measurement of unknown inductance

f (Hz)	R₀ (Ω)	$L_x = \frac{R_0}{2\pi f} \text{ (mH)}$
10000	57.5	0.915
20000	114.0	0.907
30000	105.0	0.875
		$\overline{L_X} \approx 0.899$

$$s.d._{Lx} = \sqrt{\frac{\sum_1^3 (\overline{L_x} - L_i)^2}{3}} \approx 0.017(\text{mH})$$

$$S.D._{Lx} = \frac{s.d.}{\sqrt{n}} \approx 0.009(\text{mH})$$

Result: $L_X \approx \overline{L_X} \pm \Delta L_X = 0.899 \pm 0.009 \text{ (mH)}$

2. Determination of resonant frequency of RLC circuit

a. Series RLC circuit

Trial	f_s (kHz) (series circuit)	Δf(kHz)
1	5.283	0.056
2	5.231	0.094
3	5.167	0.060
	$\overline{f} \approx 5.311(\text{kHz})$	

$$s.d. = \sqrt{\frac{\sum_1^3 (\overline{f} - f_i)^2}{3}} \approx 0.047(\text{kHz})$$

$$S.D. = \frac{s.d.}{\sqrt{n}} = \frac{0.047}{\sqrt{3}} \approx 0.027(\text{kHz})$$

Result: $f_s = \overline{f} \pm \Delta f = 5.227 \pm 0.027 \text{ (kHz)}$

b. Parallel RLC circuit

Trial	f_p (kHz) (parallel circuit)	Δf (kHz)
1	5.385	0.074
2	5.216	0.095
3	5.332	0.021
	$\bar{f} \approx 5.311$ (Hz)	

$$s.d. = \sqrt{\frac{\sum_1^3 (\bar{f} - f_i)^2}{3}} \approx 0.071 (\text{kHz})$$

$$S.D. = \frac{s.d.}{\sqrt{n}} = \frac{0.071}{\sqrt{3}} \approx 0.041 (\text{kHz})$$

$$\text{Result: } f_p = \bar{f} \pm \Delta f = 5.311 \pm 0.041 (\text{kHz})$$

***** Comparison**

Theoretical frequency:

$$\bar{f}_0 = \frac{1}{2\pi\sqrt{L_x \times C_x}} = \frac{1}{2 \times 3.14 \times \sqrt{0.899 \times 10^{-3} \times 1.024 \times 10^{-6}}} \approx 5.245 (\text{kHz})$$

From those results we have following conclusions:

- The measured frequency of parallel RLC circuit is a little bigger than those of series circuit.
- The resonant frequency is quite different from two frequencies obtain of series and parallel RLC because of low-quality equipment.