

Hanoi University of Science and Technology
School of Engineering Physics

LAB REPORT

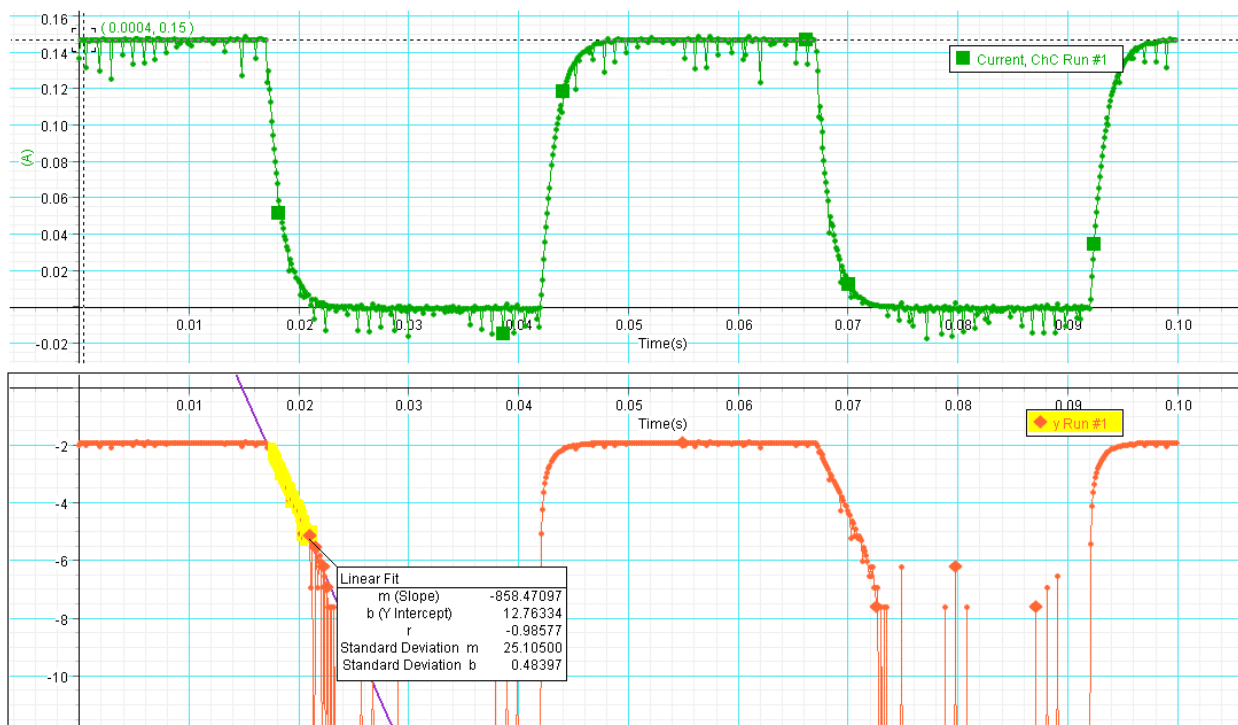
For Electrics and Thermodynamics

Experiment 3

Student name : Nguyen Viet Anh
Student ID : 20150143
Group number : 1

Experiment 3**Investigation of Electric Oscillation of RL and RLC Circuits****I. EXPERIMENTAL MOTIVATION:**

- Understanding the current across an inductor-resistor and RLC circuit, then calculate the energy of oscillation RLC circuit

II. EXPERIMENTAL RESULT**1. Resistance and Inductance of the Coil:**

(Fig1: Current in RL without core)

*** Question 1: Measure and calculate the resistance R_L of your coil L**

Input voltage is $U = 1V$.

Measured current is $I = 0.16(A)$.

⇒ Apply the Ohm's law the R_L of the coil is:

$$R_L = \frac{U}{I} = \frac{1}{0.15} = 6.67(\Omega)$$


***Question 2: Calculate the inductance of the coil without iron core base on the value of slope obtained by Data Studio software:**

By using graph, the function $\ln(i) = -(R_T/L)t + \ln(i_0)$ has a slope $m = -858.47097$;
 $\Rightarrow -(R_T/L) = -858.47097$

Then we have:

$$L_{w/c} = \frac{-R}{m} = \frac{-6.67}{-858.47097} = 7.70(mH)$$

2. Free oscillation of RLC circuit:

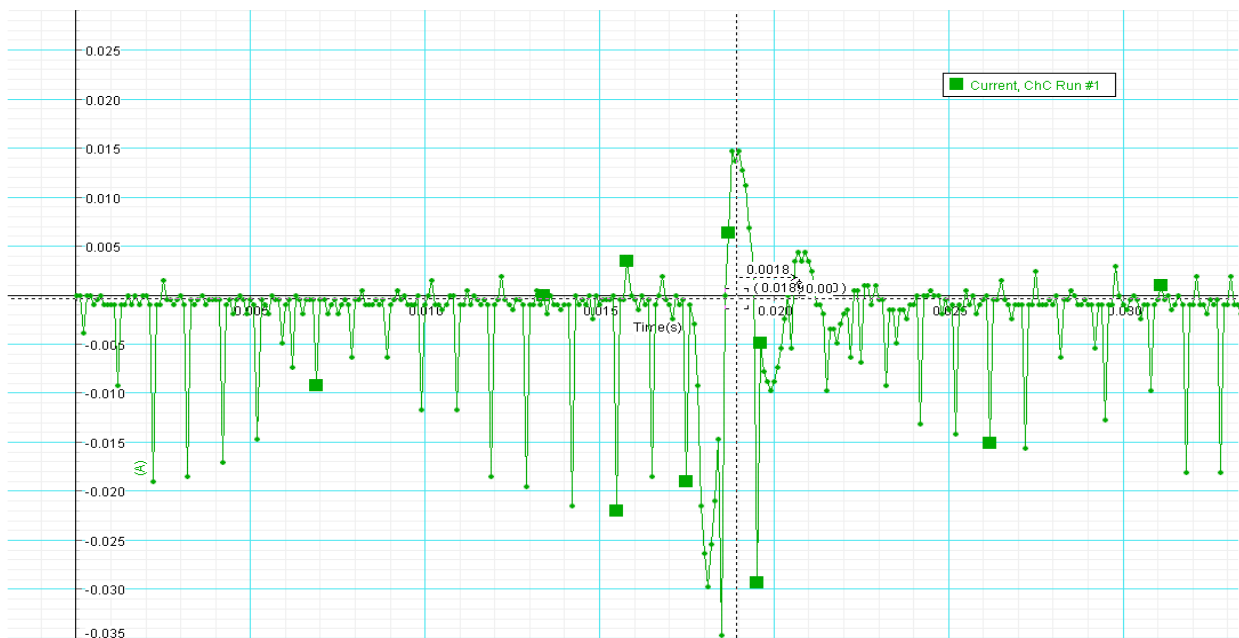

(Fig 2: Current in RLC circuit without core)

***Question 3: Calculate the frequency, $f_{measured} = 1/T(Hz)$ base on the period of oscillation determined by tools of Data Studio software**

The graph of RLC circuit without core show that the period of the RLC circuit oscillations is $T = 0.0018(s)$

Hence
$$f_{measured} = \frac{1}{T} = \frac{1}{0.0018} = 555.56(Hz)$$

***Question 4: For your circuit parameters, compute the expected value of $f_{prediction} = 1/(2\pi\sqrt{LC})$ (Hz) and compare it to your measured value. Do you expect your result to be greater, equal, or less than the measured value ($\Delta f = f_{prediction} - f_{measured}$)?**

$$f_{prediction} = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{7.7 \times 10^{-3} \times 10 \times 10^{-6}}} = 573,56(\text{Hz})$$

(as we assume the value $L = 7.7 \times 10^{-3}(\text{H})$ and $C = 10(\mu\text{F})$)

So, the expected value of f is 1 larger than the measured value amount of Δf


$$\Delta f = f_{prediction} - f_{measured} = 573,56 - 555.56 \approx 18(\text{Hz})$$

It is obvious that in the process of computing the measured value, there is the appearance of R of the coil according to the formula:

$$\omega_{w/c}^2 = \frac{1}{L_{w/c} C} - \frac{R_{total}^2}{4 L_{w/c}^2}$$

This make ω smaller \Rightarrow the frequency $f = \frac{\omega}{2\pi}$ is also smaller.

3. Observe the energy in RLC circuit:

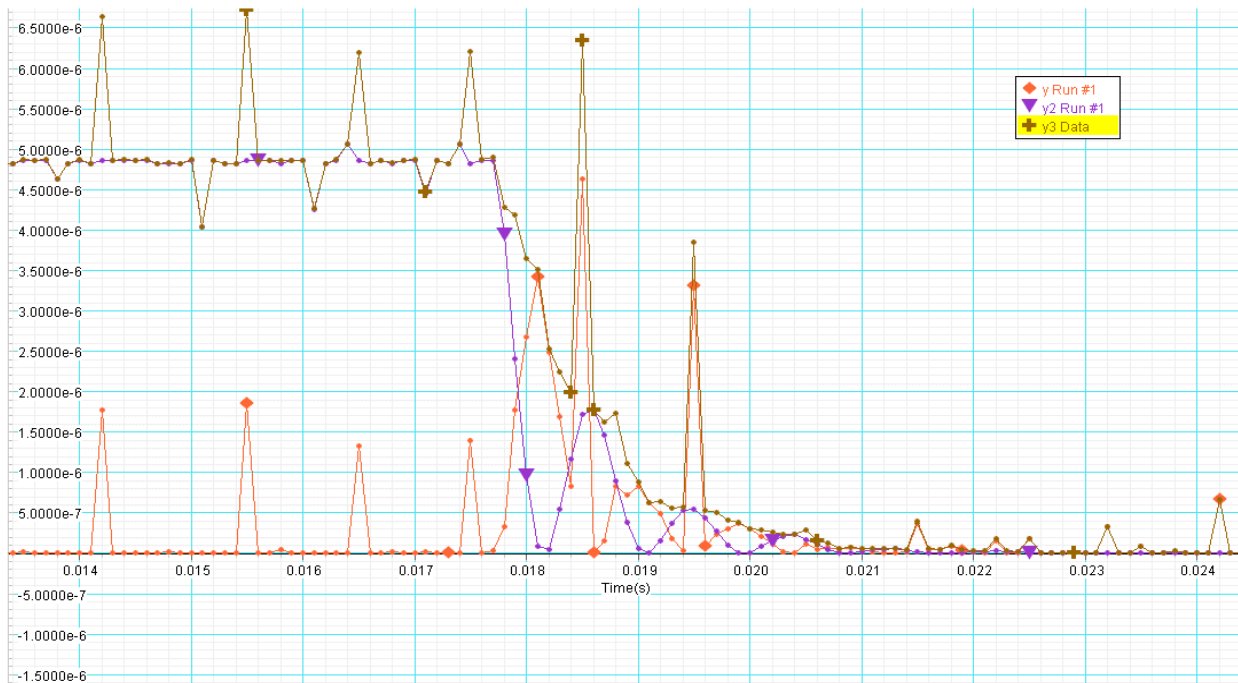

(Fig 3: energy relationship in RLC circuit)

***Question 5: The circuit is losing energy most rapidly at times when the graph of total energy is steepest; these times occur at about the same times that the magnetic energy reaches a local maximum. Briefly explain why?**

As current oscillates in RLC circuit, energy would be stored in both:

+ Magnetic field energy of inductor: $U(B) = \frac{1}{2}Li^2$

+ Electric field energy of the capacitor: $U(E) = \frac{1}{2}CV^2$

The total energy is:

$$U = U(B) + U(E) = \frac{1}{2}Li^2 + \frac{1}{2}CV^2$$

This energy lost gradually as heat in the resistor at the rate: I^2R , then over the period of oscillation T the dissipated energy is

$$\Delta U = \int_0^t I^2 R dt$$

It means that the energy in the circuit decreases faster for larger R because it disappears more rapidly into Joule heating.